

Lecture 12

ELEMENTARY QUANTUM CIRCUITS AND PROGRAMS. PART 2.

of the course “Fundamentals of Quantum Computing“

Stoyan Mishev



INSTITUTE *for* ADVANCED
PHYSICAL STUDIES



June 10, 2022

On constructing quantum circuits

Quantum Subtractor - $a - b$

Quantum Adder Modulo N - $(a + b) \bmod N$

Homework

On constructing quantum circuits

- ▶ Preparation of the input register

- ▶ Preparation of the input register
- ▶ Implementation of classical functions f by means of quantum circuits U_f on a suitable quantum register

- ▶ Preparation of the input register
- ▶ Implementation of classical functions f by means of quantum circuits U_f on a suitable quantum register
- ▶ Transformation of the quantum register by means of suitable quantum gates or circuits


- ▶ Preparation of the input register
- ▶ Implementation of classical functions f by means of quantum circuits U_f on a suitable quantum register
- ▶ Transformation of the quantum register by means of suitable quantum gates or circuits
- ▶ Reading (observing) the result in the output register

$$\begin{aligned} \boxplus : \mathbb{H}^{\otimes m} \otimes \mathbb{H}^{\otimes m} &\longrightarrow \mathbb{H}^{\otimes m} \\ |a\rangle \otimes |b\rangle &\longmapsto |a\rangle \boxplus |b\rangle := \bigotimes_{j=m-1}^0 |a_j \overset{2}{\oplus} b_j\rangle \end{aligned}$$

$$\begin{aligned} \boxplus : \mathbb{H}^{\otimes m} \otimes \mathbb{H}^{\otimes m} &\longrightarrow \mathbb{H}^{\otimes m} \\ |a\rangle \otimes |b\rangle &\longmapsto |a\rangle \boxplus |b\rangle := \bigotimes_{j=1}^m |a_j \oplus b_j\rangle \end{aligned}$$

A circuit described by the operator U_f implements the function f on $H^A \otimes H^B$ if

$$\begin{aligned} U_f : \mathbb{H}^A \otimes \mathbb{H}^B &\longrightarrow \mathbb{H}^A \otimes \mathbb{H}^B \\ |x\rangle \otimes |y\rangle &\longmapsto |x\rangle \otimes |y \boxplus f(x)\rangle \end{aligned}$$

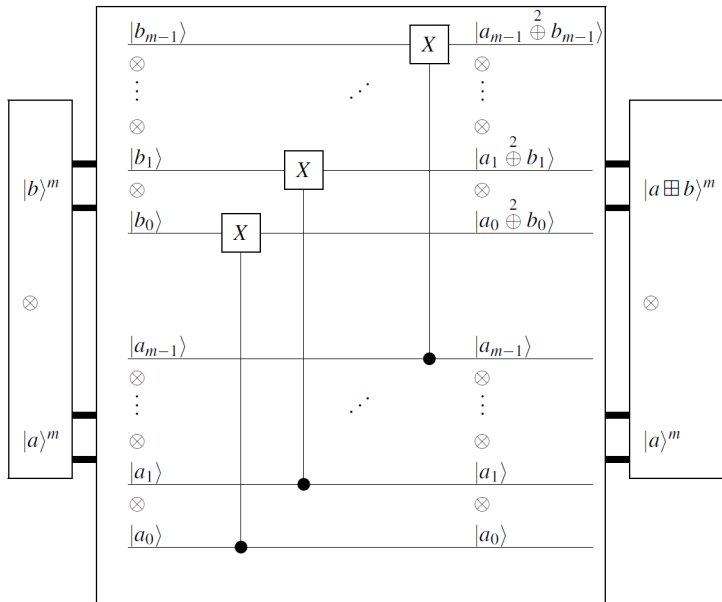

$$|\Psi_0\rangle = \frac{1}{2^{\frac{n}{2}}} \sum_{x=0}^{2^n-1} |x\rangle^n \in \mathbb{H}^{I/O}$$

$$|\Psi_0\rangle = \frac{1}{2^{\frac{n}{2}}} \sum_{x=0}^{2^n-1} |x\rangle^n \in \mathbb{H}^{I/O}$$

Hadamard gate : $H|0\rangle = \frac{|0\rangle + |1\rangle}{\sqrt{2}}$

$$|\Psi_0\rangle = \frac{1}{2^{\frac{n}{2}}} \sum_{x=0}^{2^n-1} |x\rangle^n \in \mathbb{H}^{I/O}$$

Hadamard gate : $H|0\rangle = \frac{|0\rangle + |1\rangle}{\sqrt{2}}$

$$\begin{aligned} H^{\otimes n}|0\rangle^n &= H^{\otimes n}(|0\rangle \otimes |0\rangle \otimes \cdots \otimes |0\rangle) = \bigotimes_{j=n-1}^0 H|0\rangle = \bigotimes_{j=n-1}^0 \frac{|0\rangle + |1\rangle}{\sqrt{2}} \\ &= \frac{1}{2^{\frac{n}{2}}} (|0\rangle + |1\rangle) \otimes \cdots \otimes (|0\rangle + |1\rangle) \\ &= \frac{1}{2^{\frac{n}{2}}} (\underbrace{|0\dots 0\rangle}_{=|0\rangle^n} + \underbrace{|0\dots 1\rangle}_{=|1\rangle^n} + \cdots + \underbrace{|1\dots 1\rangle}_{=|2^n-1\rangle^n}) \\ &= \frac{1}{2^{\frac{n}{2}}} \sum_{x=0}^{2^n-1} |x\rangle^n, \end{aligned}$$

A circuit described by the operator U_f implements the function f on $H^A \otimes H^B$ if

$$U_f : \mathbb{H}^A \otimes \mathbb{H}^B \longrightarrow \mathbb{H}^A \otimes \mathbb{H}^B$$
$$|x\rangle \otimes |y\rangle \longmapsto |x\rangle \otimes |y \boxplus f(x)\rangle$$

How can we do that?

A circuit described by the operator U_f implements the function f on $H^A \otimes H^B$ if

$$U_f : \mathbb{H}^A \otimes \mathbb{H}^B \longrightarrow \mathbb{H}^A \otimes \mathbb{H}^B$$
$$|x\rangle \otimes |y\rangle \longmapsto |x\rangle \otimes |y \boxplus f(x)\rangle$$

How can we do that?

1. helper gates A and B which implement f in some way non-unitarily

A circuit described by the operator U_f implements the function f on $H^A \otimes H^B$ if

$$U_f : \mathbb{H}^A \otimes \mathbb{H}^B \longrightarrow \mathbb{H}^A \otimes \mathbb{H}^B$$
$$|x\rangle \otimes |y\rangle \longmapsto |x\rangle \otimes |y \boxplus f(x)\rangle$$

How can we do that?

1. helper gates A and B which implement f in some way non-unitarily

$$A_f(|x\rangle \otimes |\omega_i\rangle) = |\psi(x)\rangle \otimes |f(x)\rangle$$
$$B_f(|\psi(x)\rangle \otimes |f(x)\rangle) = |x\rangle \otimes |\omega_f\rangle$$

A circuit described by the operator U_f implements the function f on $H^A \otimes H^B$ if

$$U_f : \mathbb{H}^A \otimes \mathbb{H}^B \longrightarrow \mathbb{H}^A \otimes \mathbb{H}^B$$

$$|x\rangle \otimes |y\rangle \longmapsto |x\rangle \otimes |y \boxplus f(x)\rangle$$

How can we do that?

1. helper gates A and B which implement f in some way non-unitarily


$$A_f(|x\rangle \otimes |\omega_i\rangle) = |\psi(x)\rangle \otimes |f(x)\rangle$$

$$B_f(|\psi(x)\rangle \otimes |f(x)\rangle) = |x\rangle \otimes |\omega_f\rangle$$

2. auxiliary qubits and circuit which uses A and B

$$\hat{U}_f := (\mathbf{1}^A \otimes S^{B,B})(B_f \otimes \mathbf{1}^B)(\mathbf{1}^A \otimes U_{\boxplus})(A_f \otimes \mathbf{1}^B)(\mathbf{1}^A \otimes S^{B,B})$$

where $S^{B,B} : |b_1\rangle \otimes |b_2\rangle \rightarrow |b_2\rangle \otimes |b_1\rangle$ is a swap operator.

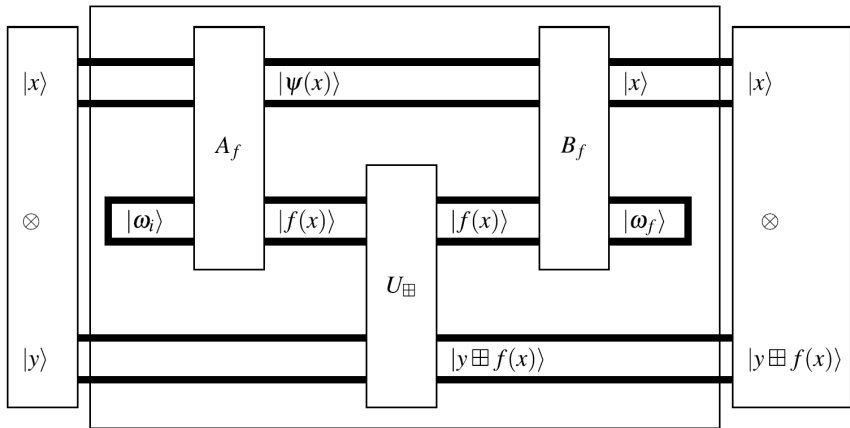

U_f

$$\begin{aligned}
& \hat{U}_f (|x\rangle \otimes |y\rangle \otimes |\omega_i\rangle) \\
& (\mathbf{1}^A \otimes S^{B,B}) (B_f \otimes \mathbf{1}^B) (\mathbf{1}^A \otimes U_{\boxplus}) (A_f \otimes \mathbf{1}^B) (|x\rangle \otimes |\omega_i\rangle \otimes |y\rangle) \\
& (\mathbf{1}^A \otimes S^{B,B}) (B_f \otimes \mathbf{1}^B) (\mathbf{1}^A \otimes U_{\boxplus}) (|\psi(x)\rangle \otimes |f(x)\rangle \otimes |y\rangle) \\
& (\mathbf{1}^A \otimes S^{B,B}) (B_f \otimes \mathbf{1}^B) (|\psi(x)\rangle \otimes |f(x)\rangle \otimes |y \boxplus f(x)\rangle) \\
& (\mathbf{1}^A \otimes S^{B,B}) (|x\rangle \otimes |\omega_f\rangle \otimes |y \boxplus f(x)\rangle) \\
& |x\rangle \otimes |y \boxplus f(x)\rangle \otimes |\omega_f\rangle.
\end{aligned}$$

Let us apply a function to the state $H^n|0\rangle$, i.e. to act on a state $H^n|0\rangle$ with H_f :

$$\begin{aligned}
 U_f|\Psi_0\rangle &= U_f((H^n|0\rangle^n) \otimes |0\rangle^m) = \frac{1}{2^{\frac{n}{2}}} \sum_{x=0}^{2^n-1} U_f(|x\rangle^n \otimes |0\rangle^m) \\
 &= \frac{1}{2^{\frac{n}{2}}} \sum_{x=0}^{2^n-1} \underbrace{|x\rangle \otimes |f(x)\rangle}_{\in \mathbb{H}^A \otimes \mathbb{H}^B}
 \end{aligned}$$

Let us apply a function to the state $H^n|0\rangle$, i.e. to act on a state $H^n|0\rangle$ with H_f :

$$\begin{aligned}
 U_f|\Psi_0\rangle &= U_f((H^n|0\rangle^n) \otimes |0\rangle^m) = \frac{1}{2^{\frac{n}{2}}} \sum_{x=0}^{2^n-1} U_f(|x\rangle^n \otimes |0\rangle^m) \\
 &= \frac{1}{2^{\frac{n}{2}}} \sum_{x=0}^{2^n-1} \underbrace{|x\rangle \otimes |f(x)\rangle}_{\in \mathbb{H}^A \otimes \mathbb{H}^B}
 \end{aligned}$$

One may take the view on this result as applying a single gate produces $2^n - 1$ values of the function at once - parallelism.

The qubits in the register can be read *independently* using the operators $\Sigma_z^j = 1^{\otimes n-1-j} \otimes \sigma_z \otimes 1^{\otimes j}$ which commute :
 $[\Sigma_z^j, \Sigma_z^i] = 0$ if $i \neq j$.


The qubits in the register can be read *independently* using the operators $\Sigma_z^j = 1^{\otimes n-1-j} \otimes \sigma_z \otimes 1^{\otimes j}$ which commute :

$$[\Sigma_z^j, \Sigma_z^i] = 0 \text{ if } i \neq j.$$

The obtained values $(s_{n-1}, \dots, s_0) \in \{\pm 1\}^n$ are stored in classical (binary) registers.

Quantum Subtractor - $a - b$

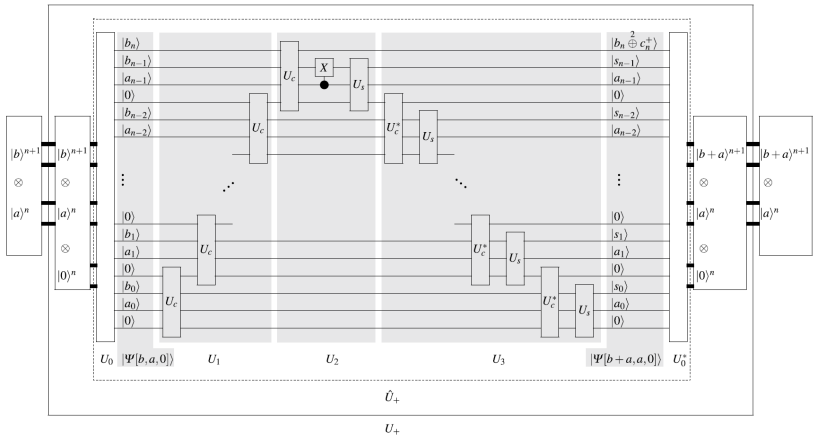if U_+ implements binary add then $U_+^{-1} \equiv U_-$ implements binary subtract !



Corollary 5.39 *There exists a circuit U_- on $\mathbb{H}^{I/O} = \mathbb{H}^B \otimes \mathbb{H}^A$, which is implemented with the help of the auxiliary register \mathbb{H}^W by $\hat{U}_+^* = \hat{U}_+^{-1}$, that is, for arbitrary $|\Phi\rangle \in \mathbb{H}^{I/O}$ one has*

$$\hat{U}_+^*(|\Phi\rangle \otimes |0\rangle^n) = (U_-|\Phi\rangle) \otimes |0\rangle^n, \quad (5.107)$$



where also $U_- = U_+^* = U_+^{-1}$ holds. Furthermore, for $a, b \in \mathbb{N}_0$ with $a, b < 2^n$ we have that



$$U_1^* U_2^* U_3^* |\Psi[b, a, 0]\rangle = |\Psi[c_n^- 2^{n+1} + b - a, a, 0]\rangle \quad (5.108)$$


$$b - a = \sum_{j=0}^{n-1} \hat{d}_j 2^j + \hat{c}_n^- 2^n$$

$$c_j^- := (1 \overset{2}{\oplus} b_{j-1}) (a_{j-1} \overset{2}{\oplus} c_{j-1}^-) \overset{2}{\oplus} a_{j-1} c_{j-1}^- \text{ for } j \in \{1, \dots, n\}$$

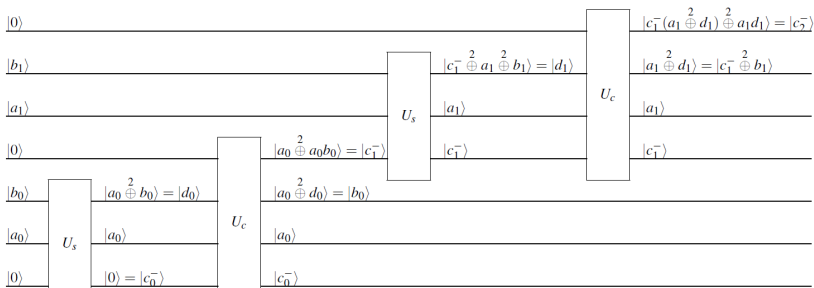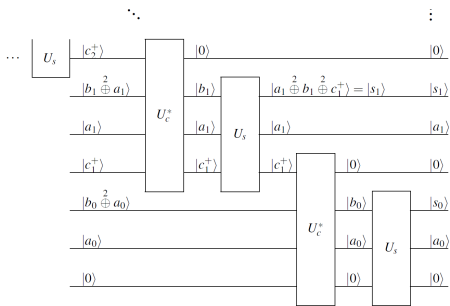
$$d_j := a_j \overset{2}{\oplus} b_j \overset{2}{\oplus} c_j^- \text{ for } j \in \{0, \dots, n-1\}.$$



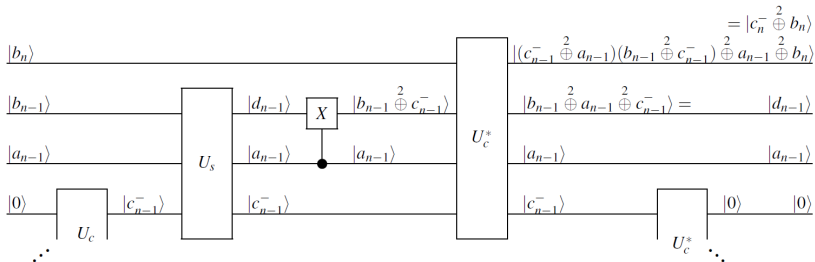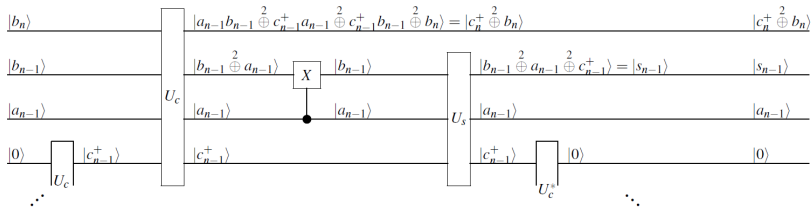

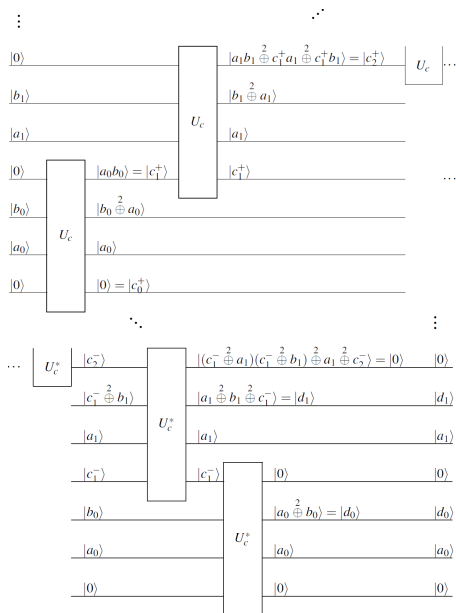

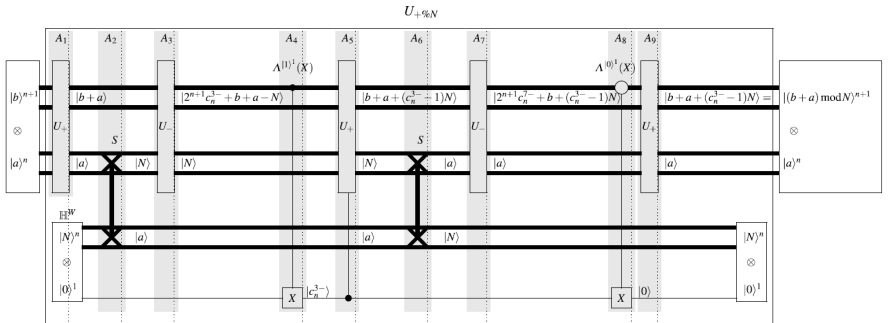Quantum Adder Modulo N - $(a + b) \bmod N$



$\mathbb{H}^W \ni 0\rangle^1$	$ 0\rangle$	$ 0\rangle$	$ 0\rangle$	$ 0\rangle$	$ 0\rangle$	$ 0\rangle$	} Target-qubit for $\Lambda^{(1)1}(X)$ in A_4 and A_8
			$ 1\rangle$	$ 1\rangle$	$ 1\rangle$	$ 0\rangle$	
b_n	c_n^{1+}	$c_n^{1-} = \begin{cases} 0 & 0 \Leftrightarrow b+a \geq N \\ 1 & 1 \Leftrightarrow b+a < N \end{cases}$	$\begin{matrix} 0 \\ 1 \end{matrix}$	$\begin{matrix} 0 \\ 0 \end{matrix}$	$\begin{matrix} c_n^{2-} = 1 \\ c_n^{2-} = 0 \end{matrix}$	$\begin{matrix} 1 \\ 0 \end{matrix}$	} Control-qubit for $\Lambda^{(1)1}(X)$ in A_4 and A_8
b_{n-1}	s_{n-1}^1	d_{n-1}^3	d_{n-1}^3	$\begin{matrix} d_{n-1}^3 \\ s_{n-1}^5 \end{matrix}$	$\begin{matrix} d_{n-1}^7 \\ b_{n-1} \end{matrix}$	$\begin{matrix} d_{n-1}^7 \\ b_{n-1} \end{matrix}$	
\vdots						\vdots	
b_1	s_1^1	d_1^3	d_1^3	$\begin{matrix} d_1^3 \\ s_1^5 \end{matrix}$	$\begin{matrix} d_1^7 \\ b_1 \end{matrix}$	$\begin{matrix} d_1^7 \\ b_1 \end{matrix}$	$\begin{matrix} (b+a-N)_{n-1} \\ (b+a)_1 \end{matrix}$
b_0	s_0^1	d_0^3	d_0^3	$\begin{matrix} d_0^3 \\ s_0^5 \end{matrix}$	$\begin{matrix} d_0^7 \\ b_0 \end{matrix}$	$\begin{matrix} d_0^7 \\ b_0 \end{matrix}$	$\begin{matrix} (b+a-N)_0 \\ (b+a)_0 \end{matrix}$

$$|b+a+(c_n^{3-}-1)N\rangle = \begin{cases} |b+a-N\rangle & \text{if } b+a \geq N \\ |b+a\rangle & \text{if } b+a < N \end{cases} = |(b+a) \bmod N\rangle$$

Homework

Write qiskit code to subtract $5 - 4$ and submit the code to `quantumcomputing@quanterall.com`

THANK YOU FOR
YOUR ATTENTION!

БЛАГОДАРЯ ЗА
ВНИМАНИЕТО!